




BITS Pilani
Pilani | Dubai | Goa | Hyderabad

Lab Assignment DEMP


S2-19 CSIWZC263/S2-19 SSWTZC263

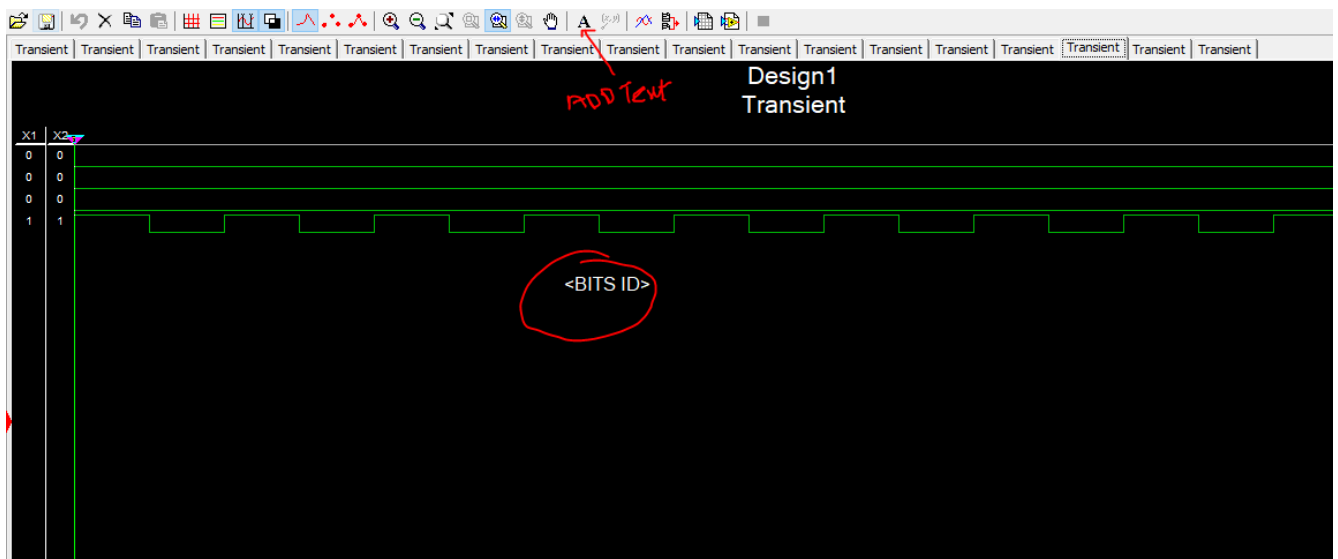Show the implementation of these circuits using Multisim and the resultant wave forms. You are required to take the screenshot of your circuit and waveform and paste it as a word file with your BITS ID mentioned on the waveform plots. The screen shot of the circuit should have the bits ID as shown. This can be done as explained below.





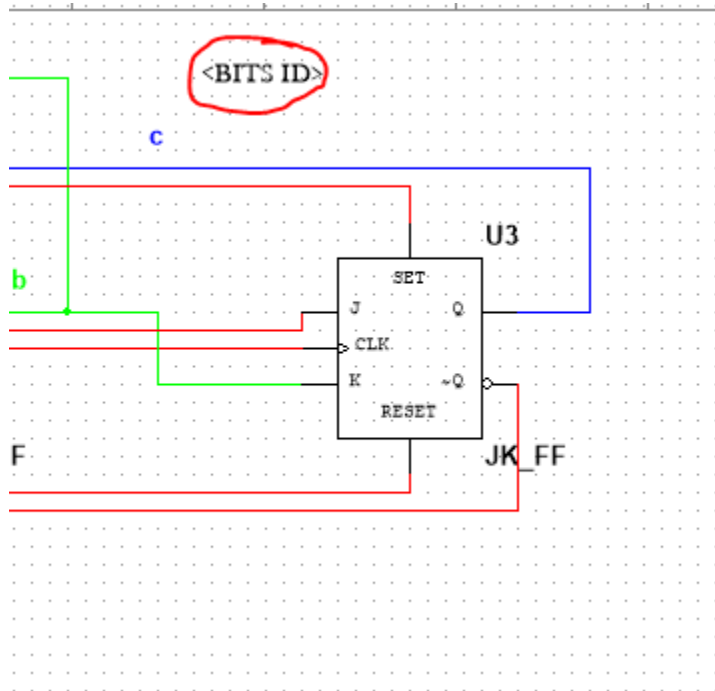For the circuit file the command is ctrl+Alt+A



Instruction:

There are two sections of the assignment.

The students are required to select two experiments from both the digital and assembly section each, and submit it on the e-learning portal. Only the assignment submitted to the e-learning portal will be evaluated. In making selection of two assignments, from the digital part, one has to select one experiment, from each of the combination and sequential part

The assignment component carries 10 marks and each question is of 2.5 marks each.

The last date of submission will be 24th September 2021, midnight

The students are advised not to wait till the last date for the submission, as there are limited number of licenses and last hour crowding may prevent from accessing the tool.

Digital Design

1. 2-bit Comparator Design a circuit that takes two unsigned 2-bit numbers (a and b), and displays one of greater($a < b$), lesser ($a < b$) or equal ($a == b$) signals.



2. Implement the function using $Y = \Sigma(1,2,3,4,6,7,9,14,15)$ the following list of components [3]

S/no	Component	quantity
1	4X1 Mux	1
2	2 input OR gates	2
3	NOT gate	2
4	2 input AND gate	1


3. Design a synchronous BCD counter using T flip flop and verify its performance using Multisim
4. Design a sequence detector circuit that produces an output pulse $z=1$ whenever the sequence 1111 appears. Overlapping sequences are accepted; for example, if the input is 01010111110 the output is 000000001110. Realise the logic using JK flip-flop, Verify the result using multisim and use four channel oscilloscope to show the waveforms as result. The waveform should include the clk, IP signal and the states of the flip-flop.

Assembly Language Programing

5. Write an assembly language program to multiply the two 16-bit words in the memory location called Multiplicand and Multiplier. The result is stored in the memory location product
6. Write an assembly language program to take average of two Number named ONE-NO and SECOND- NO and put the result in the memory location.
7. Write an assembly language program to find the LCM of Two Numbers

For all the assembly language assignment us 8086 emulator. You are required to show the following screen shots . Bits ID needs to be mentioned on all the screen shots

- a. Random access memory,

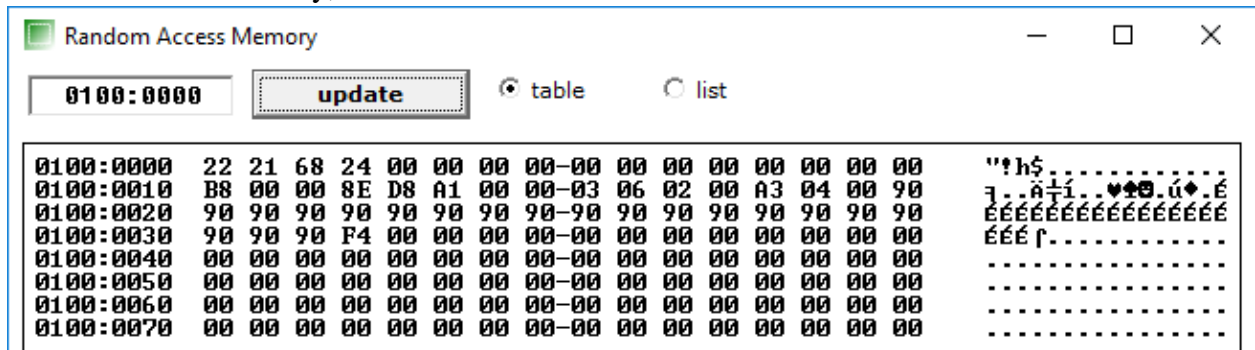



b. Flag

flags

CF	0
ZF	0
SF	0
OF	0
PF	0
AF	0
IF	1
DF	0

analyse

c. Stack

- **<ID>**

0100:FFFE	FF00	<
0100:FFFC	0000	
0100:FFFA	0000	
0100:FFF8	0000	
0100:FFF6	0000	
0100:FFF4	0000	
0100:FFF2	0000	
0100:FFF0	0000	
0100:FFEE	0000	
0100:FFEC	0000	
0100:FFEA	0000	
0100:FFE8	0000	
0100:FFE6	0000	
0100:FFE4	0000	
0100:FFE2	0000	
0100:FFE0	0000	
0100:FFDE	0000	
0100:FFDC	0000	
0100:FFDA	0000	
0100:FFD8	0000	
0100:FFD6	0000	
0100:FFD4	0000	

d. Emulator



BITS Pilani
Pilani | Dubai | Goa | Hyderabad

emulator: mycode.bin_

file debug view virtual devices virtual drive help

LOAD



reload



step back



single step



run

0

step delay ms: 0

registers

	H	L
AX	00	00
BX	00	00
CX	00	00
DX	00	00
CS	0100	
IP	0000	
SS	0100	
SP	FFFE	
BP	0000	
SI	0000	
DI	0000	
DS	0100	
ES	0100	

0100:0000

```
01000: 22 034 "
01001: 21 033 !
01002: 68 104 h
01003: 24 036 $
01004: 00 000 NULL
01005: 00 000 NULL
01006: 00 000 NULL
01007: 00 000 NULL
01008: 00 000 NULL
01009: 00 000 NULL
0100A: 00 000 NULL
0100B: 00 000 NULL
0100C: 00 000 NULL
0100D: 00 000 NULL
0100E: 00 000 NULL
0100F: 00 000 NULL
01010: B8 184 7
01011: 00 000 NULL
01012: 00 000 NULL
01013: 8E 142 ä
01014: D8 216 1/2
01015: A1 161 1
```

0100:0000

```
AND AH, [BX + DI]
PUSH 00024h
ADD [BX + SI], AL
ADD [BX + SI], AL
ADD [BX + SI], AL
ADD [BX + SI], AL
ADD [BX + SI], AL
ADD [BX + SI + 00000h], 1
MOV DS, AX
MOV AX, [00000h]
ADD AX, [00002h]
MOV [00004h], AX
NOP
NOP
NOP
NOP
NOP
NOP
NOP
NOP
NOP
...
```

screen

source

reset

aux

vars

debug

stack

flags